

COMSATS University Islamabad, Abbottabad Campus

Department of Electrical & Computer Engineering



Course Syllabus (Lab)

Digital Logic Design
CPE-241 (3+1)

BS Electrical (Computer) Engineering

1 Course Description

Introduction to Digital Computer and Systems, Number Systems, Binary Arithmetic, Boolean Algebra, Algebraic Manipulation, Canonical and Standard Form and Conversions, Logical Operations and Gates, Simplification of Functions, Karnaugh Map Methods, Two Level Implementations, Don't Care Conditions, Prime Implicants, Combinational Logic Design, Arithmetic Operations and Circuits, Analysis Procedures, Multilevel NAND/NOR Circuits, Decoders, Encoders, Multiplexers, Demultiplexers, Memory Types, Read Only Memory, Random Access Memory, Programmable Logic Array (PLA), Sequential Logic, Flip-Flops, Clocked Sequential Circuits, State Machine Concept, Design of Sequential Circuits using State Machines, Counters and their Design, Synchronous Counters, Asynchronous Counters, Shift Registers etc.

1.1 Prerequisites/Co-requisites

None

1.2 Recommended Textbook and Other Readings

1. M. Morris Mano and Charles R. Kime, Logic and Computer Design Fundamentals (2nd Edition Updated, Prentice Hall, 2000)
2. Thomas L. Floyd, Digital Fundamentals (7th Edition)

1.3 Course Requirements

1. Active COMSIS account
2. Frequent visit to COMSIS & CU portal for course updates
3. Computer resources
4. Valid CUI official email address

1.3.1 Course Contribution to Engineering:

Some of the examples and assignments require the solution of open-ended problems where the student must consider alternative solutions. In addition, they must consider economic and reliability constraints.

1.3.2 Laboratory Resources:

The Digital logic design Lab in Z block supports this class with work benches equipped with workbenches, Different Hardware equipment's Analog and Digital multimeters, logic trainers, flip flops and counters.

2 Course Learning Outcomes (CLOs) for Laboratory

After completing the course, students will be able to:

1. **Task/Practical Implementation:** Implementation of digital logic circuits (**P3-PLO5**).
2. **Punctuality and honesty :** Student is punctual, performs all the tasks and demonstrates academic honesty by refraining from all forms of plagiarism (**A3-PLO8**).
3. **Notebook reporting:** Understand and communicate the problem effectively. Comprehend and write effective reports and design documentation. Explain in one's own words the steps for performing a complex task and results/findings. (**C2-PLO10**)
4. **Problem analysis:** Analysis of logic circuits (**C4-PLO2**)
5. **Modern tool usage:** Design of logic circuits using modern tools and logic components. (**P4-PLO3**).

2.1 Standard Program Outcomes (PLOs) Addressed in Laboratory:

PLO2	Problem Analysis: An ability to identify, formulate, research literature, and analyze complex engineering problems reaching substantiated conclusions using first principle of mathematics, natural sciences and engineering sciences.
PLO3	Design/Development of Solutions: An ability to design solutions for complex engineering problems and design systems, components or processes that meet specific needs with appropriate consideration for public health and safety, cultural, societal, and environmental considerations.
PLO5	Modern Tool Usage: An ability to create, select and apply appropriate techniques, resources, and modern engineering and IT tools, including prediction and modeling, to complex engineering activities, with an understanding of the limitations.
PLO8	Ethics: Apply ethical principles and commit to professional ethics and responsibilities and norms of engineering practice.
PLO10	Communication: An ability to communicate effectively, orally as well as in writing, on complex engineering activities with engineering community and with the society at large, such as being able to comprehend and write effective reports and design documentations, make effective presentations, and give and receive clear instructions.

2.2 CLOs/PLOs Mapping

CLOs	PLOs											
	1	2	3	4	5	6	7	8	9	10	11	12
CLO 1					P3							
CLO 2								A3				
CLO 3										C2		

CLOs	PLOs											
	1	2	3	4	5	6	7	8	9	10	11	12
CLO 4		C4										
CLO 5			P4									

Knowledge Profile

2.3 Knowledge Profile (WK) Addressed in Laboratory

WK3	Theory-based engineering fundamentals
WK5	Knowledge that supports Engineering design in the practice areas
WK6	Knowledge of Engineering practice (technology) in the practice areas
WK7	Comprehension of the role of Engineering in society and identified issues in engineering practice: ethics and professional responsibility of an engineer to public safety; the impact of engineering activity: economic, social, cultural, environmental and sustainability

2.4 CLOs/WKs Mapping

CLOs	Wks							
	1	2	3	4	5	6	7	8
CLO 1						✓		
CLO 2							✓	
CLO 3								
CLO 4			✓					
CLO 5					✓			

3 Lab Report Evaluation Rubrics

3.1 Affective Level Rubrics

Criteria	Poor	Good	Very Good	Excellent	PLOs
CLO2 Punctuality and honesty	The student did not perform the given task and has poor attendance. Work is not original, and sources are not honestly cited.	Only in a few cases, student tried to perform the given task and has good attendance. For most part, work is original or taken from honestly cited sources.	Most of the time, student performs all the tasks. Attendance is very good. Work is original or taken from honestly cited sources.	The student performs all the given tasks. Attendance is excellent. Work consists of original content and /or taken from carefully cited sources.	PLO8 (Ethics)
Total point	Total Points Earned = Lab Performance Grade				100

3.2 Psychomotor Level Rubrics

Criteria	Poor	Good	Very Good	Excellent	PLOs
CLO1 Task/Practical Implementation	Student shows no response to assigned simulation and practical tasks. Participation was minimal OR student was hostile about participating.	Student can complete partial simulation and practical tasks assigned with more errors. Did the lab but did not appear very interested.	Student can complete all practical tasks assigned with less error. Used time pretty well. Stayed focused on the experiment most of the time.	Student completed all practical tasks assigned without error. Used time well in lab and focused attention on the experiment.	PLO5 (Modern Tool Usage)

Criteria	Poor	Good	Very Good	Excellent	PLOs
CLO5 Modern Tool Usage	Cannot utilize modern tools to even partially implement any desired task	Is not confident in utilization of modern tools and can only partially implement the desired task	Can confidently utilize modern tools in an effective manner to implement the desired task	Can confidently and smartly utilize modern tools in an effective, efficient manner to implement the desired task	PLO3 (Design/Development of Solutions)
Total point	Total Points Earned = Lab Performance Grade				100

3.3 Cognitive Level Rubrics

Criteria	Poor	Good	Very Good	Excellent	PLOs
CLO3 Notebook reporting	Several major aspects of the experiment are missing, student displays a lack of understanding. Very incomplete or incorrect interpretation and comparison of data indicating a lack of understanding of results.	Some of the results have been correctly interpreted and discussed; partial but incomplete understanding of results is still evident.	Important experimental details are covered, some minor details are missing. Almost all of the results have been correctly interpreted and discussed, only minor improvements are needed.	Provides all necessary background principles for the experiment. All important trends and data comparisons have been interpreted correctly and discussed, good understanding of results is conveyed.	PLO10 (Communication)

Criteria	Poor	Good	Very Good	Excellent	PLOs
CLO4 Problem analysis	Analysis is not adequate to reach even a partial (or minimal first order) solution of the problem	Partial solution is reached by a minimally adequate analysis	Complete solution is reached by a thorough analysis	Complete and optimal solution is reached by a thorough intelligent analysis that does not miss out even the fine details or any possibility for optimization	PLO2 (Problem analysis)
Total point	Total Points Earned = Lab Performance Grade				100

4 Lab Assessment Methods and Evaluation Criteria

4.1 Lab Structure

- Total 16 Lab.
- One Lab of 03 hours per week

4.2 Overall Grading Policy

Assesment Method	Marks %age
Lab Assignments/Experiments	25%
Lab Sessional 1	10%
Lab Sessional 2	15%
Lab Terminal/CEP*/Lab Project	50%
Total (Lab) 25% of course marks	100%

*For guidelines follow the CEP manual

4.3 Lab Rubrics Wiegthage

AFFECTIVE	COGNITIVE	PSYCHOMOTOR
20%	30%	50%

4.4 Mapping of CLOs to Lab Experiments

S. #	Experiment Title	CLOs				
		CLO1	CLO2	CLO3	CLO4	CLO5
Typical						
1	Introduction to the electronic workbench and logic trainer	✓	✓	✓		
2	Understanding the operation of basic logic gates (and, or, not)	✓	✓	✓		
3	Boolean analysis of logic circuits	✓	✓	✓		
4	Simplification of Boolean expressions using Boolean algebra	✓	✓	✓		
5	Implementation of Boolean functions using universal gates	✓	✓	✓		
6	Design of Adders and Subtractors	✓	✓	✓		
7	Understanding of Decoders and Encoders	✓	✓	✓		
8	Understanding of Multiplexers and Demux	✓	✓	✓		
9	Understanding and conversion of Flip-Flops	✓	✓	✓		
10	Analysis of synchronous sequential circuits	✓	✓	✓		
11	Design of synchronous sequential circuits	✓	✓	✓		
12	Design of Synchronous and Asynchronous counters	✓	✓	✓		
13	Design of Shift registers	✓	✓	✓		
Open-Ended (Suggested but not limited)						
14	OEL Sample: Implementation of higher-order Decoders	✓	✓	✓	✓	
15	OEL I: Implementation of higher-order Multiplexers	✓	✓	✓	✓	
16	OEL II: Function Implementation using Combinational circuits	✓	✓	✓	✓	
17	OEL III: Function Implementation using Sequential circuits	✓	✓	✓	✓	
18	OEL IV: Semester Project	✓	✓	✓	✓	✓

5 Lab Policy

Lab policy with regard to affective, cognitive and psychomotor learning domains will consider the following:

- Attendance is mandatory (80% minimum required).
- Students should come to the lab before the instructor. Latecomers will not be allowed to enter the lab. Students, who are absent over 25% of the class time, will not be allowed to enter the final examination.

- Students should turn off your cell phone before entering the lab. You should not leave the lab to make or take cellular phone calls.
- Students should bring a notepad and lab manual to every lab and take detailed notes and lab experiment data.
- Students should pay attention to the instructor and participate in lab discussions.
- Students should not do other work during lab time.
- Late lab assignments will not be accepted. Students who know that they are going to miss lab should plan in advance. Exams will be closed book and in-lab. There will not be any make-up for lab-session exams except the cases of hospitalization or detention
- Student should focus on technical and manipulative skills in using laboratory equipment, tools, and materials
- Student should have understanding of laboratory procedures, reporting measurements, including health & safety and scientific methods.
- Student should attain the complementary skills of collaborative learning and teamwork in laboratory settings and prepare themselves for future possible roles in laboratory base work.
- Students are required to comply with the university policy on academic integrity.
- Don't cheat. Any form of cheating, plagiarism, and/or academic dishonesty will result in an "F" grade in the course.

6 Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

TABLE OF CONTENTS

Title	Page #
1. Introduction to electronic workbench and logic trainer	3
2. Understanding the operation of basic logic gates (and, or, not)	11
3. Boolean analysis of logic circuits	21
4. Simplification of Boolean expressions using Boolean algebra	29
5. Implementation of Boolean functions using universal gates	38
6. Design of Adders and Subtractors	49
7. Understanding of Decoders and Encoders	59
8. Understanding of Multiplexers and Demux	67
9. Understanding and conversion of Flip-Flops	77
10. Analysis of synchronous Sequential circuits	87
11. Design of synchronous Sequential circuits	93
12. Design of Synchronous and Asynchronous counters	99
13. Design of Shift registers	105
OEL Sample: Implementation of higher order Decoders	110
14. OEL I: Implementation of higher order Multiplexers	113
15. OEL II: Function Implementation using Combinational circuits	117

16. OEL III: Function Implementation using Sequential circuits	121
17. OEL IV: Semester Project	125

LAB-I

INTRODUCTION TO THE ELECTRONIC WORKBENCH AND DIGITAL LOGIC TRAINER

DIGITAL LOGIC TRAINER:

INTRODUCTION:

Logic trainer is a low cost, high performance digital logic system. It is designed to provide all the basic tools necessary to conduct logic experiments.

Specifications:

- Input voltage 220V 50 Hz AC.
- Circuit type TTL compatible.
- 16 lamp monitors-transistor buffered.
- Logic probe with pulse detection.
- One clock timer.
- Output voltage +12V, -12V and +5V at 1A.

Components:

- 16 LED's with drivers.
- 8 logic switches.
- 2 logic switches with debouncing circuitry.
- Logic probe with LOW, HIGH and PULSE indicators.
- 2 push pull switches to generate negative going pulse.
- One timer based on NE-555 with variable control.
- Three 7-segment displays with BCD decoders/drivers.

- One linear variable 10K.
- One linear variable 100K.
- Two breadboards.

Power Supply:

Power supply with short circuit protection, provides +5V, +12V and -12V with power indicators and fuses. Push-in wire terminals are provided for each supply.

State Monitors:

State monitors are light emitting diodes that are used to indicate the state of a logical output. Lighted diode represents a 1 and an unlighted diode represents a 0. They are labeled L0 through L15.

Logic Switches:

Logic switches S2 through S9 are special type of switches that are designed to produce two TTL compatible logic outputs, which are complements of each other. Switches S0 and S1 are simple logic switches, each having one output and are provided with debouncing circuitry.

Digital Display:

Three 7-segment decoders/drivers and displays are provided.

Clock Timer:


A 555-clock/timer circuit is used as a pulse source. The frequency can be adjusted by turning the variable 500K pot.

ELECTRONIC WORKBENCH:

INTRODUCTION:

Electronic Workbench is a simulation package for electronic circuits. It allows to design and analyze circuits without using breadboards, real

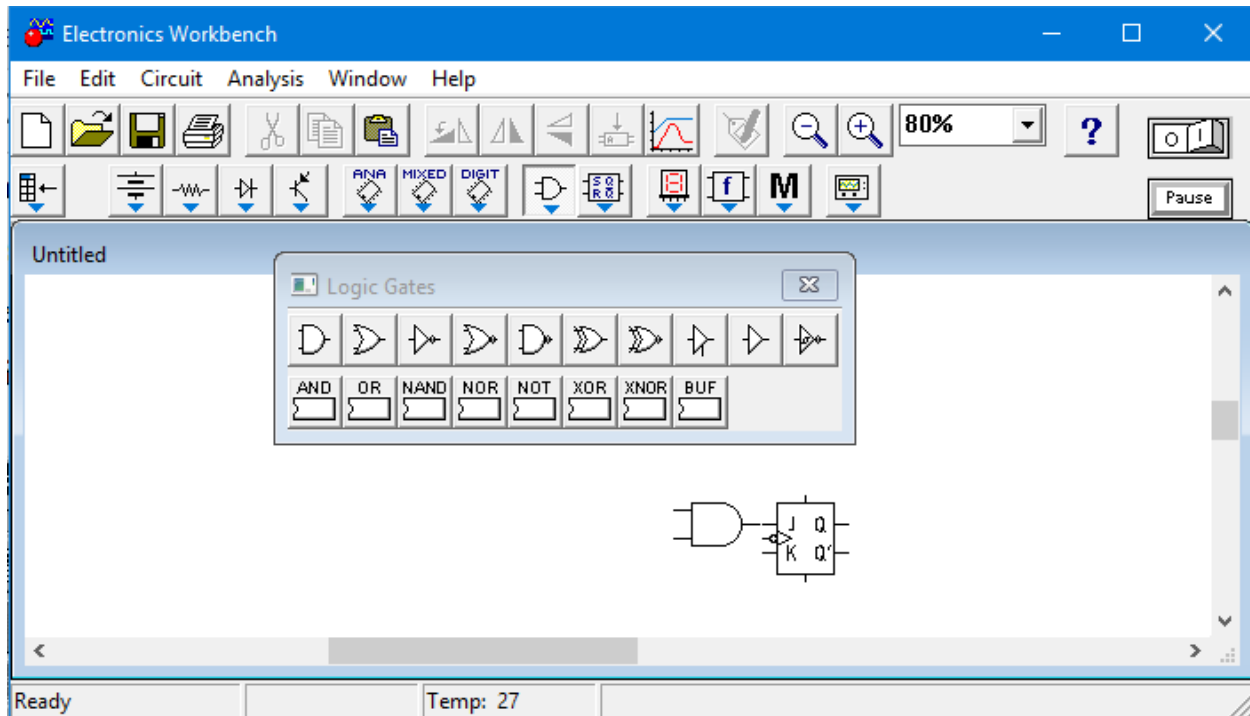components or actual instruments. EWB's click-and-drag operations make constructing and editing a circuit fast and easy. Circuit parameters and components can be changed on the fly, which makes the analysis straight forward and convenient.



GUI Interface of EWB 5.12

BASIC FUNCTIONS:

Selecting/Deselecting:

- The color of a selected component changes to red, indicating its selection.
- To select a single item, simply **click** on it.
- To select more than one items, press **CTRL+click**.
- To select all, go to **Edit>Select All** or press **CTRL+A**.
- Item(s) can also be selected by dragging the cursor.
- To deselect a single item, press **CTRL+click**.
- To deselect all, click on any empty spot inside the window.

Labeling:

To assign label to a particular component, select the component and go to ***Circuit>Component Properties..>Label***, or right click the component and go to ***Component Properties..>Label***, or simply double click the desired component.

Wiring:

To wire components together, point to the terminal of the first component, when it gets highlighted, drag the cursor to meet the terminal of the second component.

To delete a wire, select it and go to ***Edit>Delete***, or select it and press ***DEL***, or select one end of it and move it to a vacant spot on the circuit window.


To change the color of a wire, double click it, a ***Wire Properties*** pop-up window will open, where you can choose your desired color from the ***Schematic Options*** tab.

Inserting:


To insert new component into existing circuit, place it on top of the wire, it will be automatically inserted, provided there is room for it.

Simulation:

 Click the Power switch to turn power on, click it again to turn it off.




 To pause the simulation click the Pause button.




LAB TASKS:

TASK-I: Name the Basic Toolboxes of EWB

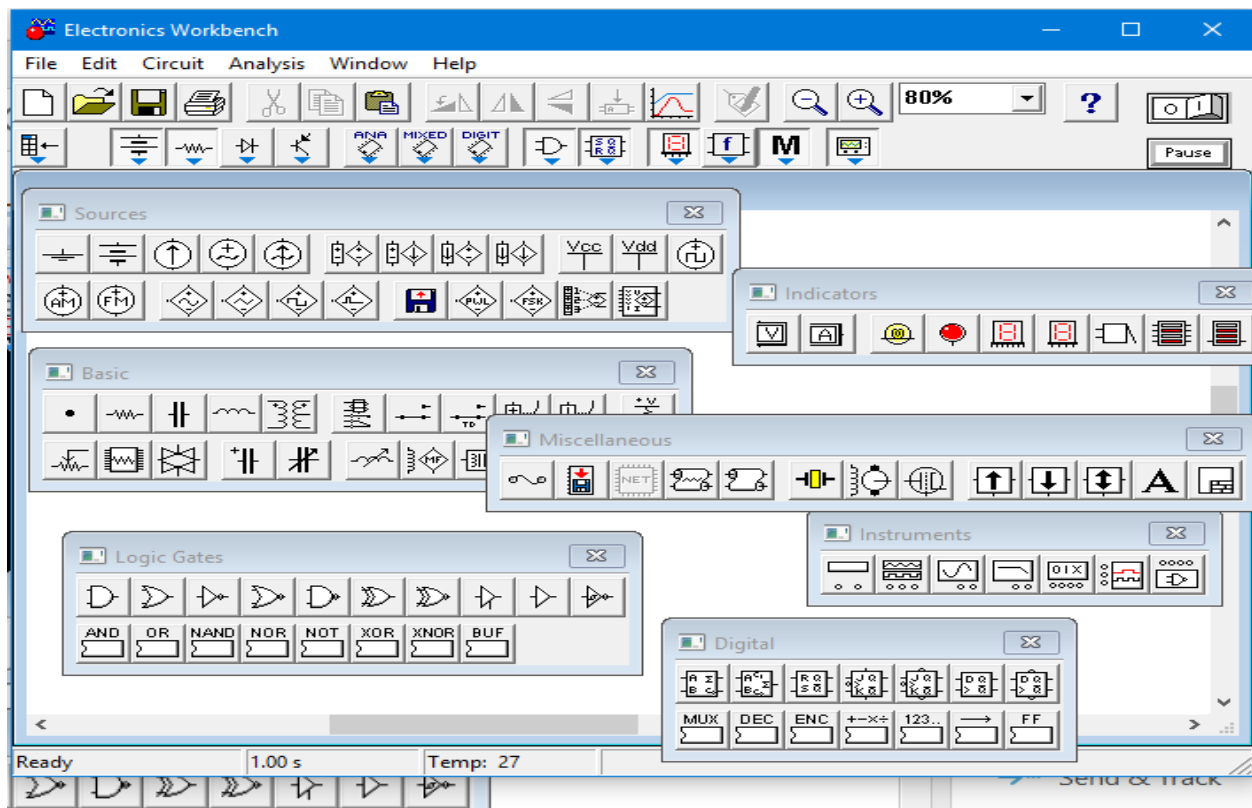

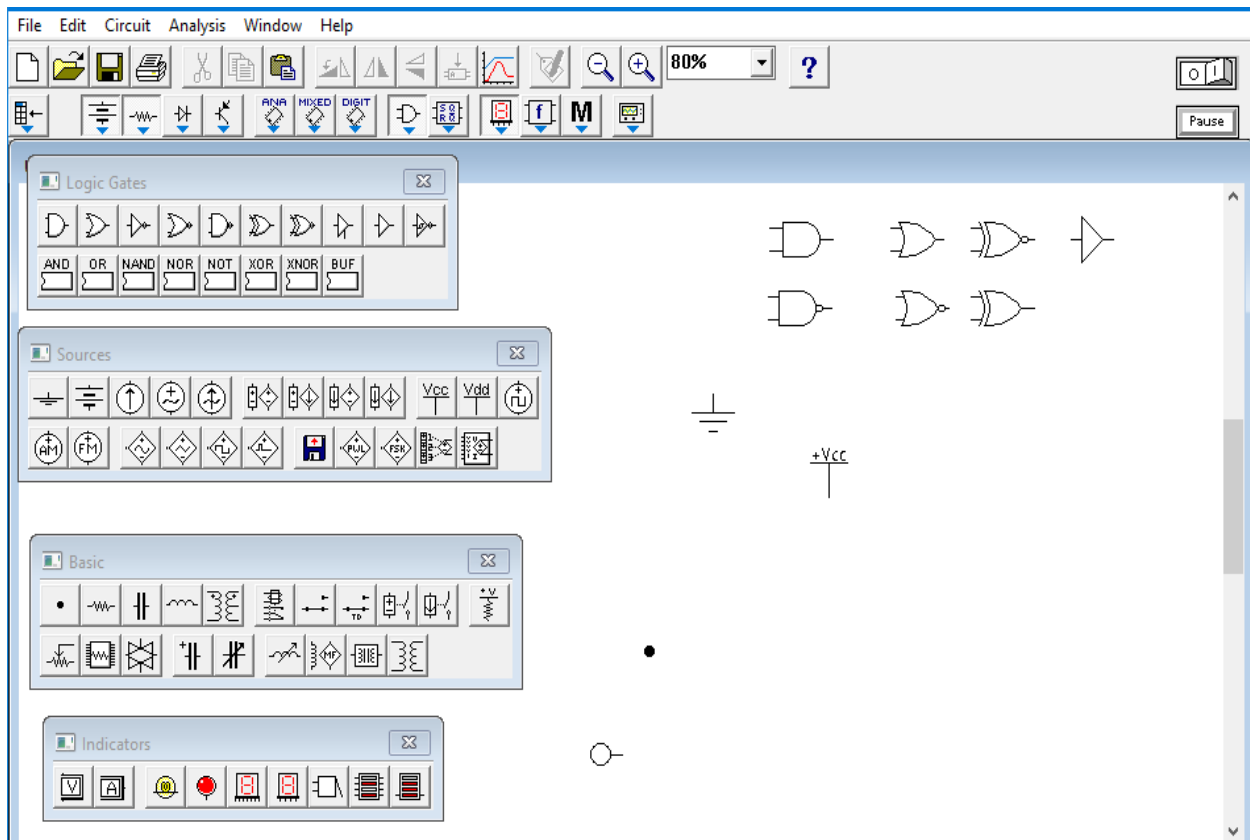TASK-II: Familiarize With Basic Buttons In EWB Toolboxes



TASK-III: Draw the following Circuit

- Connect the **Ground** to the input of the **Inverter**.
- Connect the output of the Inverter to the input of the **Red Probe**.
- Start **Simulation**.
- State your observations down.

Observations:

Stop the simulation and connect **+Vcc Voltage Source** instead of Ground to the input of the Red Probe. Start simulation and state your observations.

Observations:

TASK-IV: Name the following Icons and state down their functions









Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-II

UNDERSTANDING THE OPERATION OF BASIC LOGIC GATES (AND, OR, NOT)


OBJECTIVES:

- To study and analyze the operations of three basic logic gates (AND, OR, NOT).
- Implement them in EWB and on Logic Trainer.
- Using logic converter, derive truth tables.

INTRODUCTION:

The NOT Gate:

 
The NOT gate or Inverter performs the complementation operation. It converts 1 to 0 and 0 to 1. It has a single input and a single output. It's the only logic gate that has only one input. Logic symbol for NOT gate is shown below.



If it has A at its input, the output X will be its complement i.e. A'.

The AND Gate:

 The AND gate performs the Boolean multiplication operation. It has more than one inputs and a single output. Logic symbol for a two input AND gate is shown below.



If the two inputs are A and B, the logic expression for output X will be:


$$X = AB$$

Output of an AND gate is HIGH, if and only if all its inputs are HIGH, else the output is LOW. Truth table for a two input AND gate is shown below.

Inputs		Outputs
A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

The OR Gate:

 The OR gate performs the Boolean addition operation. It has more than one inputs and a single output. Logic symbol for a two input OR gate is shown below.



If the two inputs are A and B, the logic expression for output X will be:

$$X = A+B$$


Output of an AND gate is LOW, if and only if all its inputs are LOW, else the output is HIGH. Truth table for a two input AND gate is shown below.

Inputs		Outputs
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Pin Configuration of NOT, AND and OR ICs:


7404 (HEX INVERTER)

 - **1A, 2A, 3A, 4A, 5A, 6A:** Inputs of INV-1, INV-2, INV-3, INV-4, INV-5 and INV-6 respectively.
- **1Y, 2Y, 3Y, 4Y, 5Y, 6Y:** Outputs of INV-1, INV-2, INV-3, INV-4, INV-5 and INV-6 respectively.
- **GND and Vcc:** Supply connection lines.




7408 (Quad 2-In AND)

 - **1A and 1B:** Inputs of AND-1.
- **2A and 2B:** Inputs of AND-2.
- **3A and 3B:** Inputs of AND-3.
- **4A and 4B:** Inputs of AND-4.
- **1Y, 2Y, 3Y and 4Y:** Outputs of AND-1, AND-2, AND-3 and AND-4, respectively.
- **GND and Vcc:** Supply connection lines.



7432 (Quad 2-In OR)

 

- **1A and 1B:** Inputs of OR-1.
- **2A and 2B:** Inputs of OR-2.
- **3A and 3B:** Inputs of OR-3.
- **4A and 4B:** Inputs of OR-4.
- **1Y, 2Y, 3Y and 4Y:** Outputs of OR-1, OR-2, OR-3 and OR-4, respectively.
- **GND and Vcc:** Supply connection lines.

LAB TASKS:

TASK-I: Analyze AND, OR and NOT ICs using Logic Trainer

Analyze AND, OR and NOT ICs using logic trainer and record your observations below.

A	B	A'	B'	A + B	AB
0	0				
0	1				
1	0				
1	1				


TASK-II: Analyze AND, OR and NOT Gates in EWB


Analyze AND, OR and NOT gates (Logic Gates toolbox) by connecting their outputs to Red Probes (Indicators toolbox) and inputs to Ground and +Vcc Voltage source (Sources toolbox) independently and state your observations below.

Observations:


 
TASK-III: Find the Truth Table of a Gate using the Logic Converter

The Logic Converter can be found in the ***Instruments*** toolbox. It is used to derive a truth table from circuit schematic.




- Attach the inputs of the logic gate to the input terminals of the logic converter. There are eight input terminals on the logic converter. Use as per your need.
- Connect the output of the circuit to the single output terminal of the logic converter.
- Double click on the logic  converter, to open the logic converter display.
- Click on the circuit to truth table button.
- The truth table for the circuit will appear in the logic converter's display. The logic converter tries all possible combinations of the circuit inputs and derive its truth table.

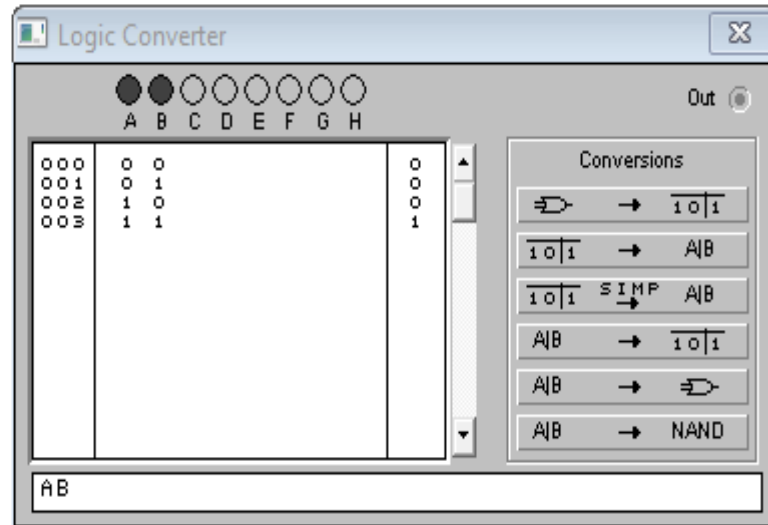 In the figure below, a two input AND gate is connected to the logic converter and its truth table is obtained. Try the same for OR and NOT gates and obtain their respective truth tables.



 TASK-IV: Find the Truth Table for the Circuit:

Using logic converter, find the truth table for the circuit below and fill the table.




A	B	$A+B$	$(A+B)'$
0	0		
0	1		
1	0		
1	1		

Note that, logic 1 means connecting the input to +Vcc Voltage Source and logic 0 means connecting the input to Ground.

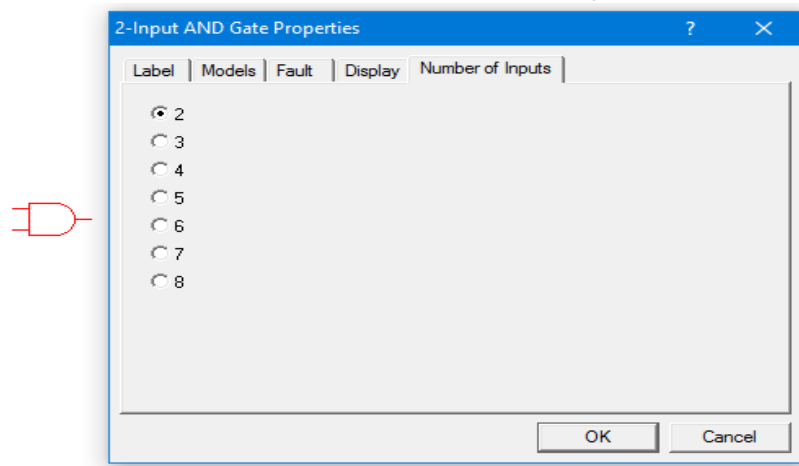TASK-V: Find the Truth Table of a Three Input Gate:

In EWB, the inputs of a gate can be changed through the following steps.

- Drag a two input gate onto the workspace in EWB.
- Double click the gate. The gate Properties dialogue box will appear.
- Click on the Number of Inputs tab and choose your desired inputs.



Using logic converter, derive the truth tables for three inputs AND and three inputs OR gates, and fill the tables below.

Inputs			Output
A	B	C	ABC
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Truth Table for a three-input AND gate

Inputs			Output
A	B	C	$A+B+C$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Truth Table for a three-input OR gate

 TASK-VI: Find the Truth Table for the Circuit:

Using logic converter, find the truth table for the circuit below.



A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor	Good	Very Good	Excellent	
		40%	50-60%	70-80%	90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-III

BOOLEAN ANALYSIS OF LOGIC CIRCUITS

OBJECTIVES:

- To convert logic circuits to Boolean expressions.
- To convert Boolean expressions to logic circuits.
- To determine truth tables for logic circuits using EWB and Logic Trainer.

INTRODUCTION:

Logic circuits are constructed from a combination of different logic gates. Boolean algebra is the mathematics of digital circuits. The operation of logic circuit can be expressed in a concise manner through Boolean algebra.





Logic can be represented in three ways.

1. Boolean Expressions
2. Boolean Circuits
3. Truth Tables

It is therefore, important to know the inter-conversion between them.

Converting Logic Circuits to Boolean Expressions:

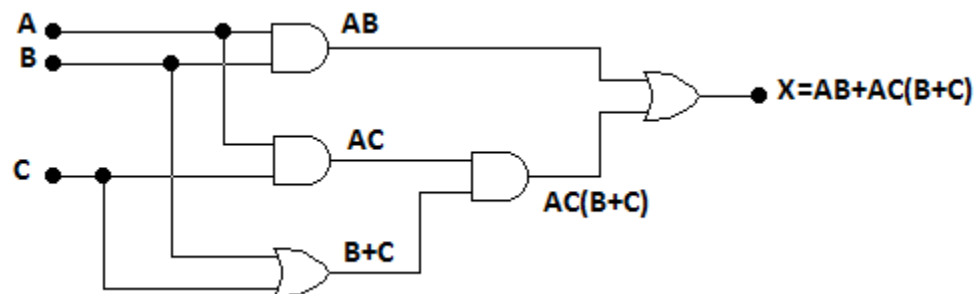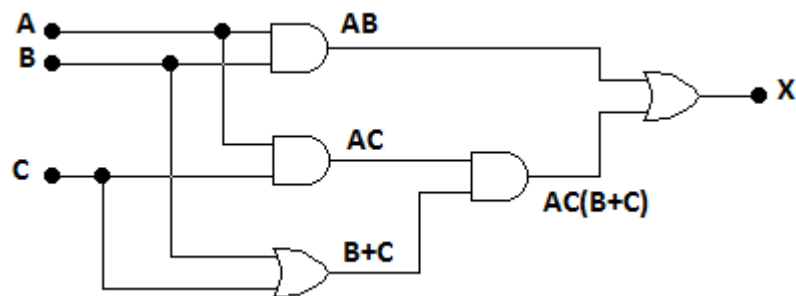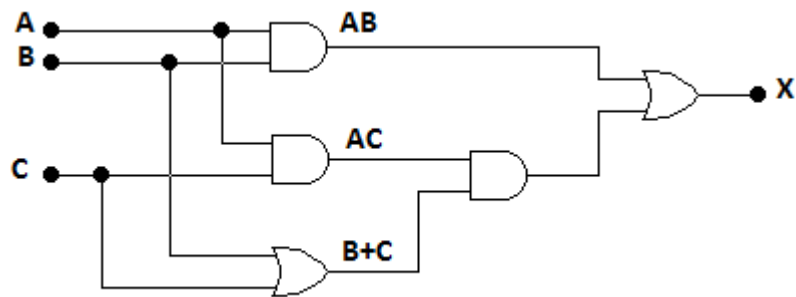 To determine Boolean expression of any logic circuit, start at the left most inputs and work towards the final output, writing logic expressions at the output of each gate, as shown below.



Converting Boolean Expressions to Logic Circuits:


To convert a Boolean expression to logic circuit, requires the knowledge of order of operation. The order of operation is as follow.

1. Bracketed quantities


2. NOTs
3. ANDs
4. ORs

Below example shows step by step conversion of Boolean expression $F = (A + BC)(A' + B)$ into logic circuit.



$$F = (A+BC)(A'+B)$$

 



$$F = (A+P)(A'+B)$$

 


$$F = Q(A'+B)$$

  

$$F = Q(R+B)$$

  


$$F = QS$$

 

LAB TASKS:

 TASK-I: Using AND, OR and NOT ICs

Use AND, OR and NOT ICs from the previous lab to implement the circuit below, using logic trainer. Record your observations in the table below and write the Boolean expression for the circuit.




A	B	C	D
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Boolean Expression: _____

 TASK-II: Finding Boolean Expressions of Logic Circuits:

Draw the circuits below on EWB, run them to fill in their respective truth tables and find the Boolean expressions of the circuits using logic converter.



Logic Circuit – I:

 


X	Y	O
0	0	
0	1	
1	0	
1	1	

Boolean Expression: _____

Logic Circuit – II

 Note: First find the truth table and Boolean function for output X and then for output Y.



A	B	C	X	Y
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Boolean Expression for X: _____

Boolean Expression for Y: _____

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-IV

SIMPLIFICATION OF BOOLEAN EXPRESSIONS USING BOOLEAN ALGEBRA

OBJECTIVES:

- To verify the rules, laws and DeMorgan's theorems of Boolean algebra using EWB and AM-2000 logic trainer.
- To simplify Boolean expressions using EWB.
- To compare original Boolean expressions with the simplified versions and to prove that they are equal using EWB and logic trainer.

INTRODUCTION:

Rules of Boolean Algebra:

Rule 1	$A + 0 = A$
Rule 2	$A + 1 = 1$
Rule 3	$A \cdot 0 = 0$
Rule 4	$A \cdot 1 = A$
Rule 5	$A + A = A$
Rule 6	$A + A' = 1$
Rule 7	$A \cdot A = A$
Rule 8	$A \cdot A' = 0$
Rule 9	$A'' = A$
Rule 10	$A + AB = A$
Rule 11	$A + A'B = A+B$
Rule 12	$(A + B)(A + C) = A + BC$

Laws of Boolean Algebra:

Commutative Laws:

Commutative Law of Addition:

$$A + B = B + A$$

Commutative Law of Multiplication:

$$A \cdot B = B \cdot A$$

Associative Laws:

Associative Law of Addition:

$$A + (B + C) = (A + B) + C$$

Associative Law of Multiplication:

$$A(BC) = (AB)C$$

Distributive Law:

$$A(B + C) = AB + AC$$

DeMorgan's Theorems:

Theorem-I: $(AB)' = A' + B'$

Theorem-II: $(A + B)' = A'B'$

Simplification of Boolean Expressions:

Simplification results in an expression with the least amount of terms having the least amount of variables in either complemented or un-complemented forms. A simplified Boolean expression results in the same output as that of the original expression but uses fewer resources (logic

gates). Thus, a simplified expression is lot more efficient and less costly to implement.

LAB TASKS:

TASK-I: Verify the Rules of Boolean Algebra:

Verify the rules of Boolean algebra in EWB and logic trainer using AND, OR and NOT ICs. Fill the tables below and state your observations.

Rule 1: $A + 0 = A$			Rule 2: $A + 1 = 1$		
A	0	$A + 0$	A	1	$A + 1$
0	0		0	1	
1	0		1	1	
Rule 3: $A \cdot 0 = 0$			Rule 4: $A \cdot 1 = A$		
A	0	$A \cdot 0$	A	1	$A \cdot 1$
0	0		0	1	
1	0		1	1	
Rule 5: $A + A = A$			Rule 6: $A + A' = 1$		
A	A	$A + A$	A	A'	$A + A'$
0	0		0		
1	1		1		

Rule 7: $A \cdot A = A$

A	A	A . A
0	0	
1	1	

Rule 9: $A'' = A$

A	A'	A''
0		
1		

Rule 11: $A + A'B = A + B$

A	B	A'	A'B	A+B	A+A'B
0	0				
0	1				
1	0				
1	1				

Observations:

Rule 8: $A \cdot A' = 0$

A	A'	A . A'
0		
1		

Rule 10: $A + AB = A$

A	B	AB	A + AB
0	0		
0	1		
1	0		
1	1		

Rule 12: $(A+B)(A+C) = A + BC$

A	B	C	A+B	A+C	BC	A+BC	(A+B)(A+C)
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

--	--

TASK-II: Verify the Laws of Boolean Algebra:

Verify the laws of Boolean algebra in EWB and logic trainer using AND, OR and NOT ICs. Fill the tables below.

Law 1.1: $A + B = B + A$

A	B	A+B	B+A
0	0		
0	1		
1	0		
1	1		

Law 1.2: $A \cdot B = B \cdot A$

A	B	AB	BA
0	0		
0	1		
1	0		
1	1		

Law 2.1: $A + (B + C) = (A + B) + C$

A	B	C	A+B	B+C	A+(B+C)	(A+B)+C
0	0	0				
0	0	1				
0	1	0				
0	1	1				

1	0	0				
1	0	1				
1	1	0				
1	1	1				

Law 2.2: $A(BC) = (AB)C$

A	B	C	AB	BC	A(BC)	(AB)C
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

Law 3: $A(B + C) = AB + AC$

A	B	C	B+C	AB	AC	A(B+C)	AB+AC
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

TASK-III: Verify DeMorgan's Theorems:

Verify DeMorgan's theorems in EWB and logic trainer using AND, OR and NOT ICs. Fill the tables below.

Theorem I: $(AB)' = A' + B'$							Theorem II: $(A + B)' = A'B'$						
A	B	A'	B'	AB	$(AB)'$	$A' + B'$	A	B	A'	B'	A+B	$(A+B)'$	$A'B'$
0	0						0	0					
0	1						0	1					
1	0						1	0					
1	1						1	1					

TASK-IV: Simplification using EWB:


Simplify the Boolean expression below, using EWB and draw its simplified circuit.


$$A(BC + B'C) + AC' + BC' + AB'C'$$

Follow the following steps:

1. Enter the Boolean expression inside the marked space on the logic converter, shown in the figure on the right.

2. Press  to obtain its truth table.

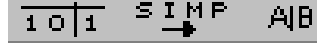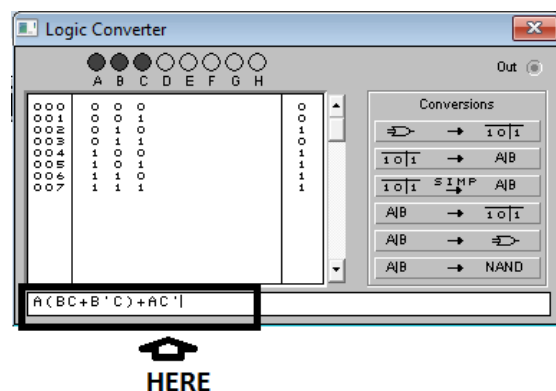3. To obtain simplified Boolean expression,  press



4. To draw the simplified circuit, press



Logic Circuit:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____: Total Marks: _____

Course Instructor: _____

LAB-V

IMPLEMENTATION OF BOOLEAN FUNCTIONS USING UNIVERSAL GATES

OBJECTIVES:

- To construct AND, OR, NOT and NOR gates using only NAND gate(s).
- To construct AND, OR, NOT and NAND gates using only NOR gate(s).
- To implement a Boolean function using only NAND gates in EWB and logic trainer.
- To implement a Boolean function using only NOR gates in EWB and logic trainer.
- To implement Boolean function with only NAND gates, using the EWB's logic converter feature.

INTRODUCTION:


Universal Gates:

NAND and NOR are referred to as universal gates, because individually both these gates can implement any Boolean function without the need to use any other type of logic gate.

NAND and NOR are both economical and easier to fabricate, compared to the rest. Because of this reason even an AND gate is typically implemented as a NAND gate followed by a NOT gate, and not the other way around. Similarly an OR gate is typically implemented as a NOR gate followed by a NOT gate, and not the other way around.

NAND Gate:

 A NAND gate has more than one input and one output. Logic symbol of a two inputs NAND gate is shown in the figure below.



If the two inputs are A and B, the Boolean expression for a NAND gate will be $(AB)'$.


The output of a NAND gate is LOW, if and only if all the inputs are HIGH, else LOW. Truth table for a two input NAND gate is given below.

A	B	$(AB)'$
0	0	1
0	1	1
1	0	1
1	1	0


According to DeMorgan's theorem:

$$(AB)' = A' + B'$$

 Hence, both NAND and Negative OR logic gates are equivalent.




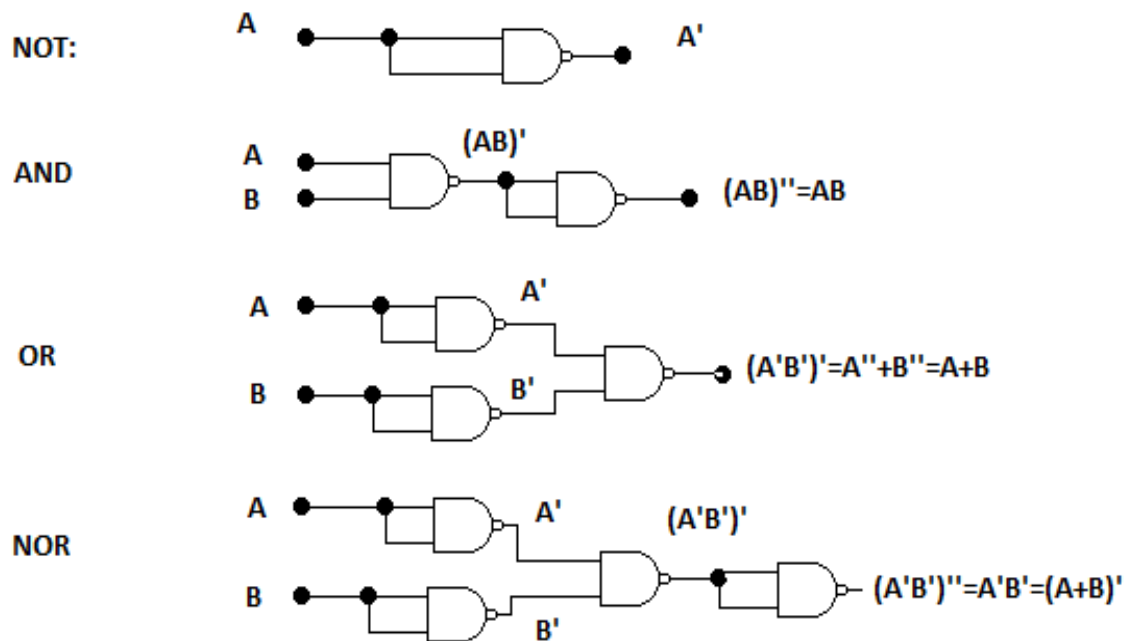Construction of NOT, AND, OR and NOR gates from NAND gate(s):



NOR Gate:

 A NOR gate has more than one input and one output. Logic symbol of a two inputs NOR gate is shown in the figure below.



If the two inputs are A and B, the Boolean expression for a NOR gate will be $(A+B)'$.

The output of a NOR gate is HIGH, if and only if all the inputs are LOW, else HIGH. Truth table for a two input NOR gate is given below.

A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0


According to DeMorgan's theorem:

$$(A+B)' = A'B'$$

Hence, both NOR and Negative AND logic gates are equivalent.



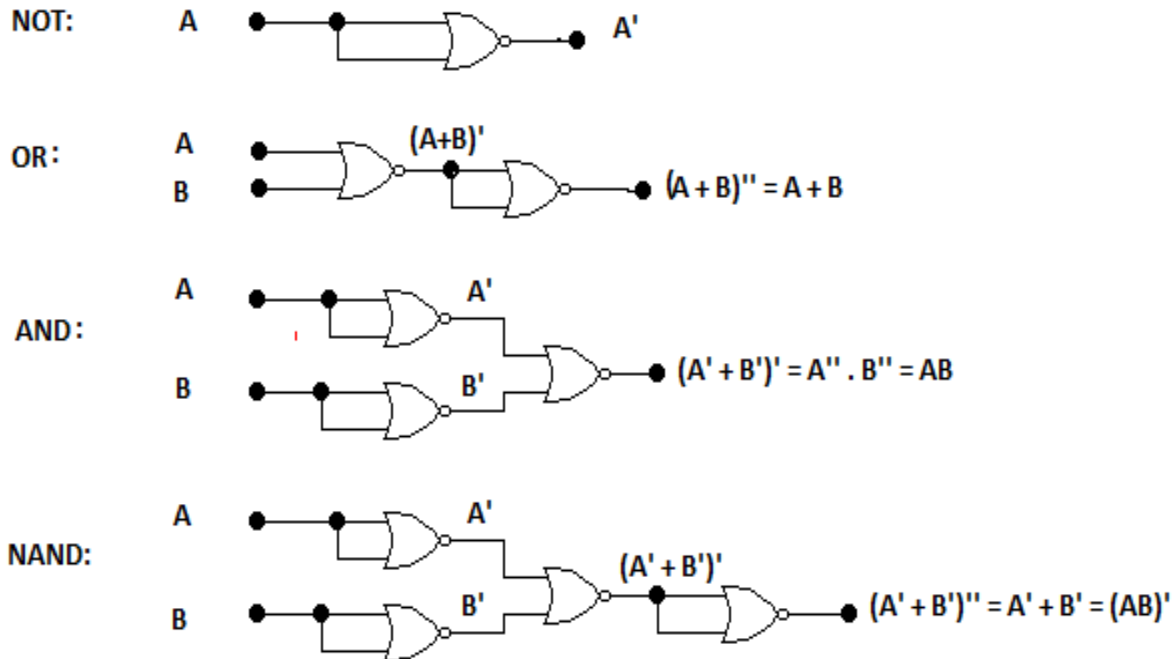Construction of NOT, OR, AND and NAND gates from NOR gate(s):



Implementation of a Two Level Boolean Function with only NAND gates:

Follow the steps below, to implement a two level Boolean function with only NAND gates.

1. Simplify the Boolean function and express it in sum of products form.
2. Draw a NAND gate, for each product term.
3. Draw a NAND gate, with inputs coming from the outputs of step-2 NAND gates.

Implementation of a Two Level Boolean Function with only OR gates:


Follow the steps below, to implement a two level Boolean function with only NOR gates.

1. Simplify the Boolean function and express it in product of sums form.
2. Draw a NOR gate, for each sum term.
3. Draw a NOR gate, with inputs coming from the outputs of step-2 NOR gates.

Pin Configuration of NAND and NOR ICs:


7400 (Quad 2-In NAND)

 - **1A and 1B:** Inputs of NAND-1.
- **2A and 2B:** Inputs of NAND-2.
- **3A and 3B:** Inputs of NAND-3.
- **4A and 4B:** Inputs of NAND-4.
- **1Y, 2Y, 3Y and 4Y:** Outputs of NAND-1, NAND-2, NAND-3 and NAND-4, respectively.
- **GND and Vcc:** Supply connection lines.



7408 (Quad 2-In AND)

 - **1A and 1B:** Inputs of NOR-1.
- **2A and 2B:** Inputs of NOR-2.
- **3A and 3B:** Inputs of NOR-3.
- **4A and 4B:** Inputs of NOR-4.
- **1Y, 2Y, 3Y and 4Y:** Outputs of NOR-1, NOR-2, NOR-3 and NOR-4, respectively.
- **GND and Vcc:** Supply connection lines.



LAB TASKS:

TASK-I: Construct NOT, AND, OR and NOR with NAND gates

Construct NOT, AND, OR and NOR gates with only NAND gates on logic trainer and fill the tables below.

NOT

A	(A.A)'
0	
1	

AND

A	B	$(AB)'$	$(AB)''$
0	0		
0	1		
1	0		
1	1		

OR

A	B	A'	B'	$(A'B')'$
0	0			
0	1			
1	0			
1	1			

NOR

A	B	A'	B'	$(A'B')'$	$(A'B')''$
0	0				
0	1				
1	0				
1	1				

TASK-II: Construct NOT, AND, OR and NAND with NOR gates

Construct NOT, AND, OR and NOR gates with only NOR gates on EWB and fill the tables below.

NOT

A	$(A+A)'$
0	
1	

OR

A	B	$(A+B)'$	$(A+B)''$
0	0		
0	1		
1	0		
1	1		

AND

A	B	A'	B'	$(A'+B')'$
0	0			
0	1			
1	0			
1	1			

NAND

A	B	A'	B'	$(A'+B')'$	$(A'+B')''$

TASK-III: Implement a Two Level Boolean Function with NAND gates

Implement the following Boolean function with only NAND gates on EWB and draw the circuit diagram.

$$F = ABC + AC + D$$

Circuit Diagram:

TASK-IV: Implement a Two Level Boolean Function with NOR gates

Implement the following Boolean function with only NOR gates on logic trainer and draw the circuit diagram.

$$F = ABC + AC + D$$

Circuit Diagram:

TASK-V: Implement a Boolean Function with NAND gates, using Logic Converter

Implement the function below with NAND gates using the EWB's logic converter and draw the circuit diagram.

$$F = A(B'C + C') + BC' + A$$

Write the Boolean expression in the logic trainer and press button.



Circuit Diagram:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-VI

DESIGN OF ADDERS AND SUBTRACTORS

OBJECTIVES:

- To design half adder and full adder.
- To design half subtractor and full subtractor.
- To design a parallel binary adder.

INTRODUCTION:

Half Adder:

A half adder accepts two bits at its inputs and produces two outputs, sum and carry-out. Truth table of a half adder is as follow.

Truth Table:

Inputs		Outputs	
A	B	S	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Boolean Functions:

$$S = A'B + AB' = A \oplus B$$

$$C_{out} = AB$$

Full Adder:

A full adder accepts three bits at its inputs and produces two outputs, sum and carry-out. Truth table of a full adder is as follow.

Truth Table:

Inputs			<u>Outputs</u>	
A	B	C	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Functions:

$$S = A'B'C + A'BC' + AB'C' + ABC$$

$$S = (A'B' + AB) C + (A'B + AB') C'$$

$$S = (A \oplus B)' C + (A \oplus B) C'$$

$$\mathbf{S = (A \oplus B) \oplus C}$$

$$C_{out} = A'BC + AB'C + ABC' + ABC$$

$$C_{out} = (A'B + AB') C + AB (C' + C)$$

$$\mathbf{C_{out} = (A \oplus B) C + AB}$$

Half Subtractor:

A half subtractor accepts two bits at its inputs and produces two outputs, difference and borrow-in. Truth table of a half subtractor is as follow.

Truth Table:

Inputs		Outputs	
A	B	D	B _{in}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Boolean Functions:

$$D = A'B + AB' = A \oplus B$$

$$B_{in} = A'B$$

Full Subtractor:

A full subtractor accepts three bits at its inputs and produces two outputs, difference and borrow-in. Truth table of a full subtractor is as follow.

Truth Table:

Inputs			Outputs	
A	B	C	D	B _{in}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Boolean Functions:

$$D = A'B'C + A'BC' + AB'C' + ABC$$

$$D = (A'B' + AB) C + (A'B + AB') C'$$


$$D = (A \oplus B)' C + (A \oplus B) C'$$

$$D = (A \oplus B) \oplus C$$

$$\text{Bin} = A'B'C + A'BC' + A'BC + ABC$$

$$\text{Bin} = (A'B' + AB) C + A'B (C' + C)$$

$$\text{Bin} = (A \oplus B)' C + A'B$$

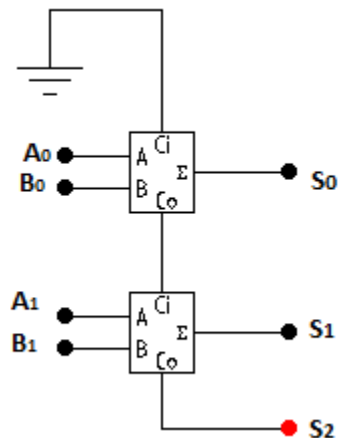


Parallel Binary Adder:

Two or more full adders are connected to form a parallel binary adder. In the figure on the right a 2-bit parallel binary adder is drawn by connecting two full adders. The 2-bit parallel binary adder can add two 2-bit numbers.

Pin Configuration of XOR IC:

7486 (Quad 2-In XOR)

- Pin description is self-explanatory.

 

LAB TASKS:

TASK-I: Implement Half Adder

Implement half adder on logic trainer. Use AND and XOR gates and draw

Logic Circuit:

the logic circuit below.

TASK-II: Implement Half Adder

Implement full adder on logic trainer. Use NOT, AND, OR and XOR gates and draw the logic circuit below.

Logic Circuit:

TASK-III: Implement Half Subtractor

Logic Circuit:


Implement half subtractor on logic trainer and draw the logic circuit.

TASK-IV: Implement Full Subtractor

Logic Circuit:

Implement full subtractor on logic trainer and draw the logic circuit.

TASK-V: Design a Four Bit Parallel Binary Adder:

Design a four bit parallel binary adder using the digital toolbox  of EWB to add two 4-bit binary numbers. Draw the logic diagram below.

Logic Diagram:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____: Total Marks: _____

Course Instructor: _____

LAB-VII

UNDERSTANDING OF DECODERS AND ENCODERS

OBJECTIVES:


- To understand the operations of 2 x 4, 3 x 8 and 4 x 16 decoders.
- To implement Boolean functions using decoders.
- To understand the operations of encoders.

INTRODUCTION:


Decoder:

A decoder detects the presence of a specific combinations of bits at its inputs and indicates their presence by a specific voltage levels at its outputs. If a decoder has n input lines, it can have 1 to 2^n output lines.

Truth table, block diagram and logic diagram of a 2 x 4 decoder (active-LOW outputs) are shown below.

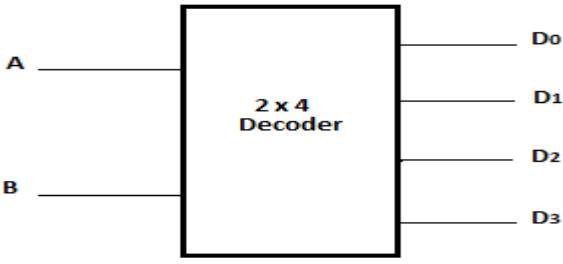Truth Table:						Block Diagram:			
Inputs		Outputs							
A	B	D ₀	D ₁	D ₂	D ₃				
0	0	0	1	1	1				
0	1	1	0	1	1				
1	0	1	1	0	1				
1	1	1	1	1	0				

Logic Diagram:

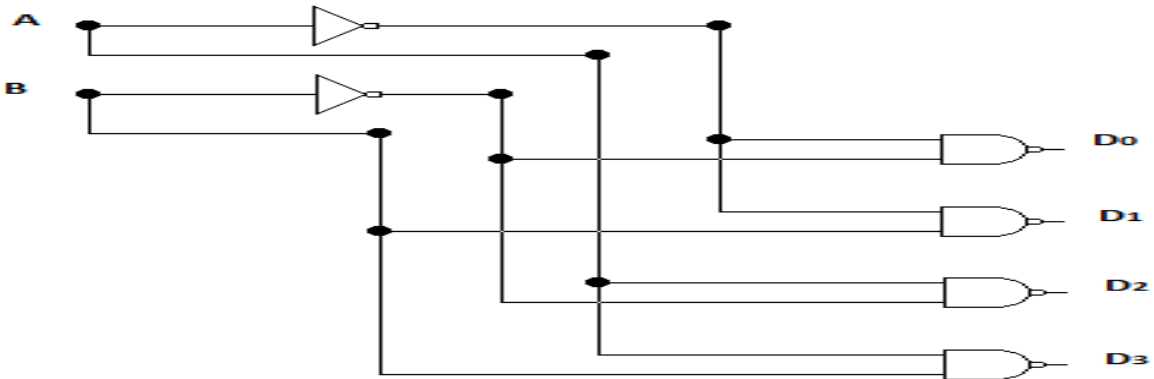


Boolean Function Implementation using Decoder:

Follow the following procedure to implement a Boolean function using decoder.

- The Boolean function must be in standard SOP form. If it is not, convert it to standard SOP.
- Choose a decoder that has the same inputs as the number of variables in the domain of the Boolean function.
- According to the min terms in the Boolean function, choose the decoder outputs and feed them to a NAND gate if the decoder is active LOW, or OR gate if it is active HIGH.

Example:

$$F_{(A,B,C)} = \sum (0,4,6,7)$$

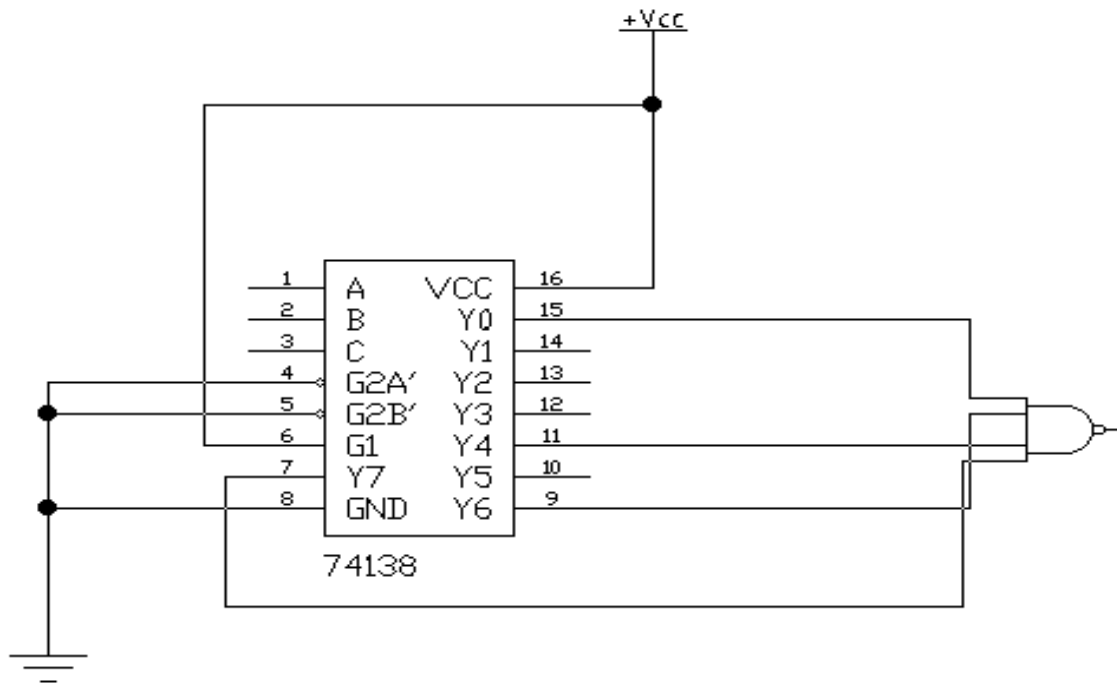


Pin Configuration of Decoder/DEMUX ICs:

74139:

74139 is a dual 2 x 4 Decoder/DEMUX. It has two decoders/DEMUX, one on the either side. Pin description is as follows.

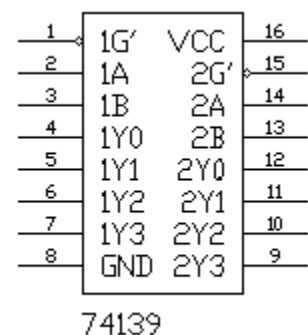- **1A and 1B:** Input/select lines for decoder/DEMUX 1, where 1A is the LSB and 1B is the MSB.
- **2A and 2B:** Input/select lines for decoder/DEMUX 2, where 2A is the LSB and 2B is the MSB.
- **1Y0 through 1Y3:** Active low data outputs of decoder/DEMUX 1.
- **2Y0 through 2Y3:** Active low data outputs of decoder/DEMUX 2.




- **1G'**: Active low enable input for decoder/DEMUX 1.
- **2G'**: Active low enable input for decoder/DEMUX 2.
- **VCC and GND**: Supply connection lines.

74138:

74138 is a 3 x 8 Decoder IC. Pin description is as follows.

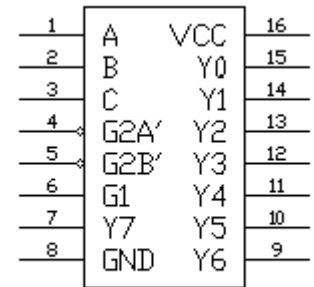- **A, B and C**: Input/select lines with A being the LSB and C being the MSB.
- **Y0 through Y7**: Active low data outputs.
- **G2A' and G2B'**: Active low enable inputs.
- **G1**: Active high enable input.
- **VCC and GND**: Supply connection lines.




74138

74154:

74154 is a 4 x 16 Decoder IC. Pin description is as follows.

 - **A, B, C and D**: Input/select lines with A being the LSB and D being the MSB.
- **0 through 15**: Active low data outputs.
- **G1' and G2'**: Active low enable inputs.
- **VCC and GND**: Supply connection lines.



74154

LAB TASKS:

TASK-I: Implement a 3 x 8 Decoder:

Implement a 3 x 8 decoder on logic trainer and fill the table below.

Inputs			Outputs							
A	B	C	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

TASK-II: Implement Full adder using Decoder and NAND gate:

Implement full adder using a decoder and NAND gate on EWB and draw the logic diagram below.

Logic Diagram:

TASK-III: Implement DECIMAL to BCD encoder using 74HC147:

Draw the PIN configuration of 74HC147



Truth
DECIMAL to BCD encoder.

table for

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-VIII

UNDERSTANDING OF MULTIPLEXERS AND DEMUX

OBJECTIVES:

- To understand the operation of multiplexers.
- To implement Boolean functions using multiplexer.

INTRODUCTION:

Multiplexer:

A multiplexer has multiple inputs, single output and data select lines. The number of data select lines depends on the number of input lines. For 2^n input lines, we require n data select lines. The data select lines decide which input's line data should be transmitted on the single output line, as shown in the table below. In the block diagram, S0 and S1 are data select lines, A, B, C and D are data input lines and Y is the output line.

Block Diagram:

 


Table:


Data Sect Lines		Output Line
S ₁	S ₀	Y
0	0	A
0	1	B
1	0	C
1	1	D

Output Function:

The output function for 4 x 1 multiplexer is,

$$Y = AS_1'S_0' + BS_1'S_0 + CS_1S_0' + DS_1S_0$$

which can be implemented as below.

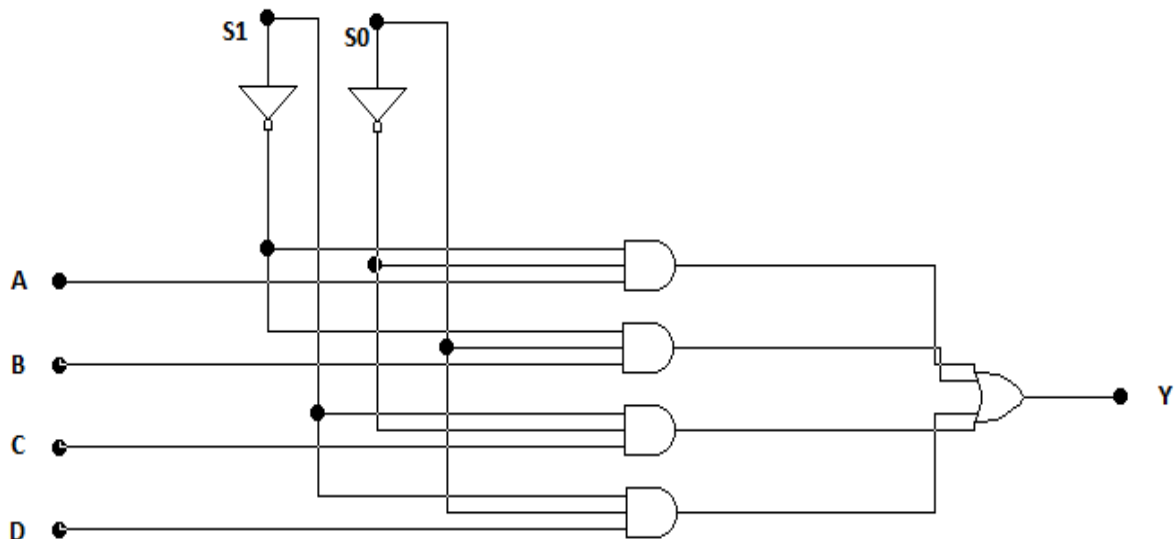Logic Diagram:**Boolean Function Implementation:**

To implement Boolean function using multiplexer, follow the steps below.

- Express the Boolean function in standard SOP form.
- Choose a multiplexer that has one less data select line than the number of variables in the domain of the Boolean function.
- Construct a truth table for the Boolean function.
- Connect the most significant variables of the Boolean function with the data select lines of the multiplexer.

- Express the output as a function of the least significant variable, for every unique combination of other variables in the truth table, and apply them to the data input lines of multiplexer.


Example:

$$F(A,B,C) = \sum(1,2,6,7)$$

A	B	C	F	F in terms of C
0	0	0	0	F = C
0	0	1	1	
0	1	0	1	F = C'
0	1	1	0	
1	0	0	0	F = 0
1	0	1	0	
1	1	0	1	F = 1
1	1	1	1	

Truth Table of the Boolean function

Implementation of Boolean Function

 


Pin Configuration of Multiplexer ICs:

74153:

74139 is a dual 4 x 1 Multiplexer IC. It has two 4 x 1 Multiplexers, one on the either side. Pin description is as follows.

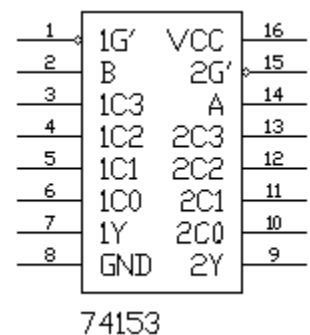
- **1C0, 1C1, 1C2 and 1C3:** Data input lines for MUX-I.
- **2C0, 2C1, 2C2 and 2C3:** Data input lines for MUX-II.
- **1Y:** Output for MUX-I.
- **2Y:** Output for MUX-II.
- **A and B:** Data select lines, with A being the LSB.
- **1G':** Active low enable input for MUX-I.
- **2G':** Active low enable input for MUX-II.
- **VCC and GND:** Supply connection lines.



74151:

74151 is a 8 x 1 Multiplexer IC. Pin description is as follows.

 
- **A, B and C:** Data select lines with A being the LSB.
- **D0 through D7:** Data input lines.
- **Y:** Active high output.
- **W:** Active low output.
- **G':** Active low enable input.
- **VCC and GND:** Supply connection lines.



74154:

74150 is a 16 x 1 Multiplexer IC. Pin description is as follows.

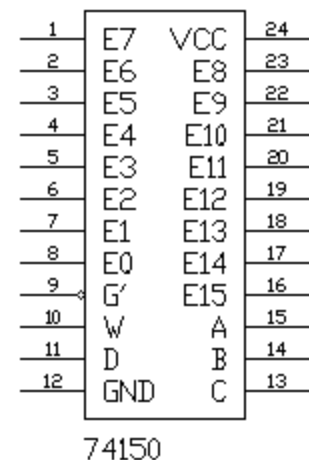- **A, B, C and D:** Data select lines with A being the LSB.
- **E0 through E15:** Data input lines.
- **G1':** Active low enable input.
- **W:** Active low output.
- **VCC and GND:** Supply connection lines.



LAB TASKS:

TASK-I: Implement the Boolean Function:

Implement the Boolean function below, using appropriate multiplexer IC, on logic trainer and fill the table.

$$F(A,B,C) = \sum(0, 1, 2, 7)$$

A	B	C	F	F in terms of C
0	0	0		F =
0	0	1		
0	1	0		F =
0	1	1		
1	0	0		F =
1	0	1		
1	1	0		F =
1	1	1		

TASK-II: Implement the Boolean Function:

Implement the Boolean function below, using appropriate multiplexer IC, on EWB and fill the table.

$$F(A,B,C) = \sum(1, 3, 6, 7)$$

A	B	C	F	F in terms of C
0	0	0		F =
0	0	1		
0	1	0		F =
0	1	1		
1	0	0		F =
1	0	1		
1	1	0		F =
1	1	1		

TASK-III: Implement the Boolean Function:

Implement the Boolean function below, using appropriate multiplexer IC, on EWB and fill the table and draw the logic diagram.


$$F(A,B,C,D) = \sum(1, 5, 9, 10, 11, 14)$$

A	B	C	D	F	F in terms of C
0	0	0	0		F =
0	0	0	1		
0	0	1	0		F =
0	0	1	1		
0	1	0	0		F =
0	1	0	1		
0	1	1	0		F =
0	1	1	1		
1	0	0	0		F =
1	0	0	1		
1	0	1	0		F =
1	0	1	1		
1	1	0	0		F =
1	1	0	1		
1	1	1	0		F =
1	1	1	1		

Logic Diagram:

TASK-IV: Implement of DEMUX using DECODER:

Draw the PIN configuration of 74HC154

 

Truth table for Demux using 74HC154 decoder.

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-IX

UNDERSTANDING AND CONVERSION OF FLIP-FLOPS

OBJECTIVES:

- To understand the operations of different flip-flops.
- To convert one type of flip-flop into another.

INTRODUCTION:

Flip-Flop:

Flip-flop is the memory unit or storage element of synchronous sequential circuit. It can store one bit of information, either 1 or 0 at a time. A 1 means that the sequential circuit is in the SET state and a 0 means that it is in the RESET state.

A flip-flop can be either positive edge triggered or negative edge triggered. A positive edge triggered flip-flop changes state only, when the clock pulse goes from LOW to HIGH. A negative edge triggered flip-flop changes state only, when the clock pulse goes from HIGH to LOW.

The next state (Q_{t+1}) of flip-flop, is not only defined by the flip-flop inputs but also by the present state (Q_t) of the storage element.

Different Types of Flip-Flops:

S-R Flip-Flop:

S-R flip-flop has two inputs, S and R and two outputs Q and Q'. Q is the normal output and Q' is the complemented output. The characteristic table and characteristic equation of S-R flip-flop is given below.

Characteristic Table:

S	R	Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x

Characteristic Equation:

$$Q_{t+1} = S + R'Q_t$$

D Flip-Flop:

D flip-flop has one input, D and two outputs Q and Q'. Q is the normal output and Q' is the complemented output. The characteristic table and characteristic equation of D flip-flop is given below.

Characteristic Table:

D	Q_t	Q_{t+1}
0	0	0
0	1	0
1	0	1
1	1	1

Characteristic Equation:

$$Q_{t+1} = D$$

J-K Flip-Flop:

J-K flip-flop has two inputs, J and K and two outputs Q and Q'. Q is the normal output and Q' is the complemented output. The characteristic table and characteristic equation of J-K flip-flop is given below.

Characteristic Table:				Characteristic Equation: $Q_{t+1} = JQ_t' + K'Q_t$
J	K	Q_t	Q_{t+1}	
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	0	

D Flip-Flop:

T flip-flop has one input, T and two outputs Q and Q'. Q is the normal output and Q' is the complemented output. The characteristic table and characteristic equation of T flip-flop is given below.

Characteristic Table:				Characteristic Equation: $Q_{t+1} = T \oplus Q_t$
T	Q_t	Q_{t+1}		
0	0	0		
0	1	1		
1	0	1		
1	1	0		

Conversions of Flip-Flops:

Using a conversion table, one flip-flop can be converted into another.

A conversion table has three main columns.

- The input(s) of the flip-flop to which the original flip-flop needs to be converted, constitutes the first main column.
- The outputs, both the present state Q_t and next state Q_{t+1} , constitutes the second main column.
- The input(s) of the original flip-flop constitutes the third main column.

The number of inputs in the first column along with the present state Q_t , defines the total number of possible combinations in the conversion table.

For each combination, find the next state Q_{t+1} values and then using the information in the second main column fill the third main column.

Finally, find the simplified Boolean function(s) for each entity in the third main column and implement it.

Example: Conversion of S-R flip-flop to J-K flip flop

Conversion Table:

Inputs of J-K Flip-Flop		Outputs		Inputs of S-R Flip-Flop	
J	K	Q_t	Q_{t+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

Obtaining Boolean Functions:


J \ KQt				
	00	01	11	10
0	0	X	0	0
1	1	X	0	1

$$S = JQt'$$

J \ KQt				
	00	01	11	10
0	X	0	1	X
1	0	0	1	0

$$R = KQt$$


Logic Diagram:

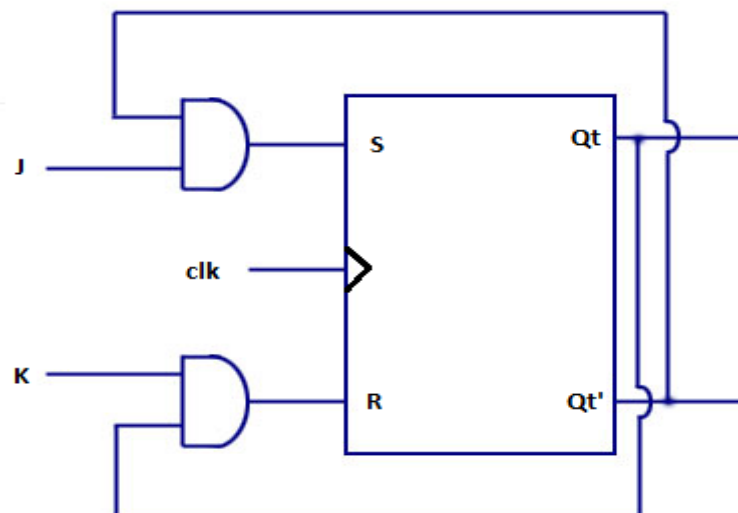

Pin Configurations of Different Flip-Flop ICs:


Pin description is self-explanatory.

7473 (Dual JK FF (clr))

 


7473


7474 (Dual D type FF (pre, clr))

 


7474

 7476 (Dual JK FF (pre, clr))


7476

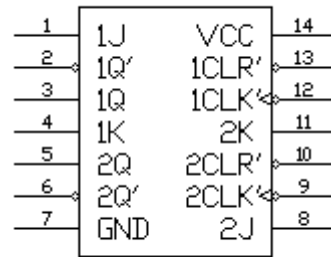74107 (Dual JK FF (clr))

74107

 74109 (Dual JK FF (+edge, pre, clr))

74109

 74112 (Dual JK FF (-edge, pre, clr))

74112

LAB TASKS:

TASK-I: Use 74109 (Dual JK FF (+edge, pre, clr)) IC to fill the table below:

J	K	Clk	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	

1	1	0	
1	1	1	

TASK-II: Use 74112 (Dual JK FF (+edge, pre, clr)) IC to fill the table below:

J	K	Clk	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

TASK-III: Convert J-K to S-R

Convert J-K flip-flop to SR flip-flop. Fill the conversion table below. Write Boolean functions for J and K and draw the logic diagram.

Conversion Table:

Inputs of S-R Flip-Flop		Outputs		Inputs of J-K Flip-Flop	
J	K	Qt	Qt+1	S	R
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			

1	0	1			
1	1	0			
1	1	1			

Boolean Functions:

Logic Diagram:

TASK-IV: Convert D to J-K

Logic Diagram:

Convert D flip-flop to J-K flip-flop, and draw the logic diagram below.

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-X

ANALYSIS OF SYNCHRONOUS SEQUENTIAL CIRCUITS

OBJECTIVE:

- To analyze synchronous sequential circuits.

INTRODUCTION:

Synchronous Sequential Circuits:

Sequential circuits that are synchronized with a clock are referred to as synchronous or clocked sequential circuits. They are characterized by inputs, outputs and states. Outputs and next states are both, functions of inputs and present states.

The memory or storage element used in a synchronous sequential circuit is a flip-flop.

Analysis of Synchronous Sequential Circuits:

There are three ways to analyze a synchronous sequential circuit.

- Algebraic Analysis.
- Tabular Analysis.
- Graphical Analysis.

Algebraic Analysis:

Algebraic analysis of synchronous sequential circuit is performed using State Equations. A state equation defines the next state as a function of both the inputs and present states.

Tabular Analysis:

Tabular analysis of synchronous sequential circuit is performed using State Table. A state table is similar to a truth table. The input portion of state table consists of external inputs to the sequential circuit and present states. Next states and circuit outputs comprise the output portion.

There are four main columns in a state table, present states, inputs, next states and outputs. The number of rows in a state table depend on the combined total number of external inputs and present states.

Graphical Analysis:

Graphical analysis of synchronous sequential circuit is performed using State Diagrams. In a state diagram, a state is represented by a circle and the transition from one state to another is indicated by an arrow. Inputs and outputs are listed over the arrow in the form **(x/y)**, where x is an input and y is an output. Multiple inputs and multiple outputs are separated by **commas**.

Flip-Flop Input Function: It is the Boolean function that represent input to a flip-flop, in terms of present states and external input(s).

Circuit Output Function: It is the Boolean function that represent output of the sequential circuit, in terms of present states and external input(s).

Analysis Procedure:


- Find the flip-flop inputs and circuit output functions
- Obtain state equations, by substituting flip-flop input functions into flip-flop characteristic equations.
- Use the state equations and circuit output functions to fill the next state and output columns of state table.

- Graphically represent state table by means of state diagrams.

LAB TASKS:

Analyze a Synchronous Sequential Circuit

 Analyze the synchronous sequential circuit below, by first implementing it on logic trainer and then find its state equations, state table and state diagram.



Flip-Flop Input Functions: $J_A =$ _____ $K_A =$ _____ $J_B =$ _____ $K_B =$ _____**Circuit Output Function:** $Y =$ _____**State Equations:** $A_{t+1} =$ _____

 $B_{t+1} =$ _____

State Table:

Present States		Input	Next States		Output
A	B	X	A	B	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

State Diagram:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-XI

DESIGN OF SYNCHRONOUS SEQUENTIAL CIRCUITS

OBJECTIVE:

- To design synchronous sequential circuits.

INTRODUCTION:

Synchronous Sequential Circuits:

Sequential circuits that are synchronized with a clock are referred to as synchronous or clocked sequential circuits. They are characterized by inputs, outputs and states. Outputs and next states are both, functions of inputs and present states.

The memory or storage element used in a synchronous sequential circuit is a flip-flop.


Design Procedure:

- Obtain state table from the word description or state diagram, whichever is provided.
 - Reduce the state table.
 - Assign binary values to each state.
 - Derive a circuit excitation and output table.
 - Find the minimized flip-flop input and circuit output functions.
 - Draw the logic diagram.
-

LAB TASKS:

Design a Synchronous Sequential Circuit

 Design a synchronous sequential circuit, using J-K flip-flops from the state diagram given below.



State Table:

Present State	Next State x = 0	Next State x = 1	Output x = 0	Output x = 1
a				
b				
c				
d				
e				
f				

Reduced State Table:

Present State	Next State $x = 0$	Next State $x = 1$	Output $x = 0$	Output $x = 1$

State Assignment:

Present States		Next State $x = 0$		Next State $x = 1$		Output $x = 0$	Output $x = 1$
A	B	A	B	A	B	y	y
0	0						
0	1						
1	0						
1	1						

Circuit Excitation and Output Table:

Inputs of Combinational Circuit			Next States				Outputs of Combinational Circuit				
Present States		Inputs	$x = 0$		$x = 1$		FF Inputs				Output
A	B	x	A	B	A	B	JA	KA	JB	KB	y
0	0	0									
0	0	1									
0	1	0									

0	1	1									
1	0	0									
1	0	1									
1	1	0									
1	1	1									

Flip-Flop Input Functions (minimized):

$J_A =$ _____

$K_A =$ _____


$J_B =$ _____

$K_B =$ _____

Circuit Output Function:

$Y =$ _____

Logic Diagram:

 

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-XII

DESIGN OF SYNCHRONOUS AND ASYNCHRONOUS COUNTERS

OBJECTIVES:

- To design different types of counters.

INTRODUCTION:

Counters:

Counters are synchronous sequential circuits that are used for counting purposes. The total number of flip-flops in a counter determine the total number of states that the counter goes through. A counter goes through 2^n states, if the total number of flip-flops used are n . The arrangement of flip-flops and the combinational logic used in a counter determine the sequence of counting operation.

Counters can be classified as synchronous or asynchronous counters.

Synchronous Counters:

In a synchronous counter, all the flip-flops within the counter are synchronized with a single clock pulse.

Asynchronous Counters:

In asynchronous counter, flip-flops within the counter have different clock pulses.

Some common terminologies, related with counters are listed below.

Binary Counter: A counter that follows the binary sequence of counting.

Binary UP Counter: A binary counter, whose count sequence goes from the least significant value to the most significant value.

Binary DOWN Counter: A binary counter, whose count sequence goes from the most significant value to the least significant value.

Binary UP/DOWN Counter: A binary counter, which is capable of counting both in the UP as well as in the DOWN direction.

Modulus: Modulus of a counter is the total number of states that the counter goes through.

Maximum Modulus: Maximum modulus is the maximum number of states that a counter can go through.

Truncated Sequence: Truncated sequence is the sequence of states of a counter, whose modulus is less than the maximum modulus.

Decade Counter: A truncated sequence counter whose modulus is 10 is referred to as a decade counter.

BCD Counter: Example of decade counter.

LAB TASKS:

TASK-I: Design a Synchronous UP Counter

Design a 3-bit synchronous UP counter, using J-K flip-flops on logic trainer. Fill the table and draw the logic diagram below. In the table Q_A is the LSB and Q_C is the MSB.

Clock Pulse	Q_C	Q_B	Q_A
0			
1			
2			
3			

4			
5			
6			
7			
8			

Logic Diagram:

TASK-II: Design Asynchronous DOWN Counter

Design a 3-bit asynchronous DOWN counter, using J-K flip-flops on logic trainer. Fill the table and draw the logic diagram below. In the table Q_A is the LSB and Q_C is the MSB.

Clock Pulse	Q_C	Q_B	Q_A
0			
1			
2			
3			
4			
5			
6			
7			
8			

Logic Diagram:

TASK-III: Design a Binary Counter

Design a binary counter that goes through the following states, using J-K flip-flops and draw the logic diagram. Use the unused states as don't cares. In the table below, Q_A is the LSB and Q_C is the MSB.

Clock Pulse	Q_C	Q_B	Q_A
0	0	0	0
1	0	0	1
2	0	1	1
3	1	0	1
4	1	1	0
5	1	1	1

Logic Diagram:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

LAB-XIII

DESIGN OF SHIFT REGISTERS

OBJECTIVES:

- To design different types of registers.

INTRODUCTION:

Registers:

Registers have two basic functions.

- Data Storage
- Data Movement

The storage capacity of a register depends on the total number of flip-flops used in its design. A register with n flip-flops can store a maximum of n bits.

Depending on the type of data movement, a register can be classified into;

- Serial-In, Serial-Out Register
- Serial-In, Parallel-Out Register
- Parallel-In, Serial-Out Register
- Parallel-In, Parallel-Out Register
- Bidirectional Shift Register
- Universal Shift Register

Serial-In, Serial-Out Register:

In serial-in, serial-out register, the data bits are entered serially (right most bit first) and are taken out serially.

Serial-In, Parallel-Out Register:

In serial-in, parallel-out register, the data bits are entered serially (right most bit first) and are taken out simultaneously in a parallel manner.

Parallel-In, Serial-Out Register:

In parallel-in, serial-out register, the data bits are entered simultaneously and are taken out in a bit by bit fashion.

Parallel-In, Parallel-Out Register:

In parallel-in, parallel-out register data bits are loaded simultaneously as well as taken out simultaneously.

Bidirectional Shift Register:

In bidirectional shift register, that data is loaded serially and taken out serially like a serial-in, serial-out register, but the data can move in either direction from left to right or from right to left.

Universal Shift Register:

In universal shift register, the data can be loaded both simultaneously or bit by bit. Similarly the data can be taken out in either simultaneous manner or bit by bit fashion. The data bits can also move in either direction that is from left to right or from right to left.

LAB TASKS:

TASK-I: Design a three bit serial-in, serial-out register

Using D flip-flops ICs, design a 3-bit serial-in, serial-out register on logic trainer.

Serially input 0111001 with the right most bit first and record your observations below. Also draw the logic diagram.

Clock Pulse	Q _A	Q _B	Q _C
0	0	0	0
1			
2			
3			
4			
5			
6			
7			

Logic Diagram:

TASK-II: Design a three bit serial-in, parallel-out register

Using D flip-flops ICs, design a 3-bit serial-in, parallel-out register on logic trainer.

Serially input 0111001 with the right most bit first and record your observations on the 1st, 5th and 7th clock pulse below. Also draw the logic diagram.

Clock Pulse	Q_A	Q_B	Q_C
0	0	0	0
1			
5			
7			

Logic Diagram:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

OEL - SAMPLE

IMPLEMENTATION OF HIGHER ORDERS DECODERS

OBJECTIVES:

- To implement higher order decoders from lower order decoders.
- To implement Boolean functions using decoders.

INTRODUCTION:

Decoder:


A decoder detects the presence of a specific combinations of bits at its inputs and indicates their presence by a specific voltage levels at its outputs. If a decoder has n input lines, it can have 1 to 2^n output lines.

Pin Configuration of Decoder/DEMUX ICs:

74139:

74139 is a dual 2 x 4 Decoder/DEMUX. It has two decoders/DEMUX, one on the either side. Pin description is as follows.

 - **1A and 1B:** Input/select lines for decoder/DEMUX 1, where 1A is the LSB and 1B is the MSB.
- **2A and 2B:** Input/select lines for decoder/DEMUX 2, where 2A is the LSB and 2B is the MSB.
- **1Y0 through 1Y3:** Active low data outputs of decoder/DEMUX 1.




74139

- **2Y0 through 2Y3:** Active low data outputs of decoder/DEMUX 2.
- **1G':** Active low enable input for decoder/DEMUX 1.
- **2G':** Active low enable input for decoder/DEMUX 2.
- **VCC and GND:** Supply connection lines.

Implementing Higher Order Decoder from Lower Order Decoders:

 In the figure below a 3 x 8 decoder is implemented using three 2 x 4 decoders.




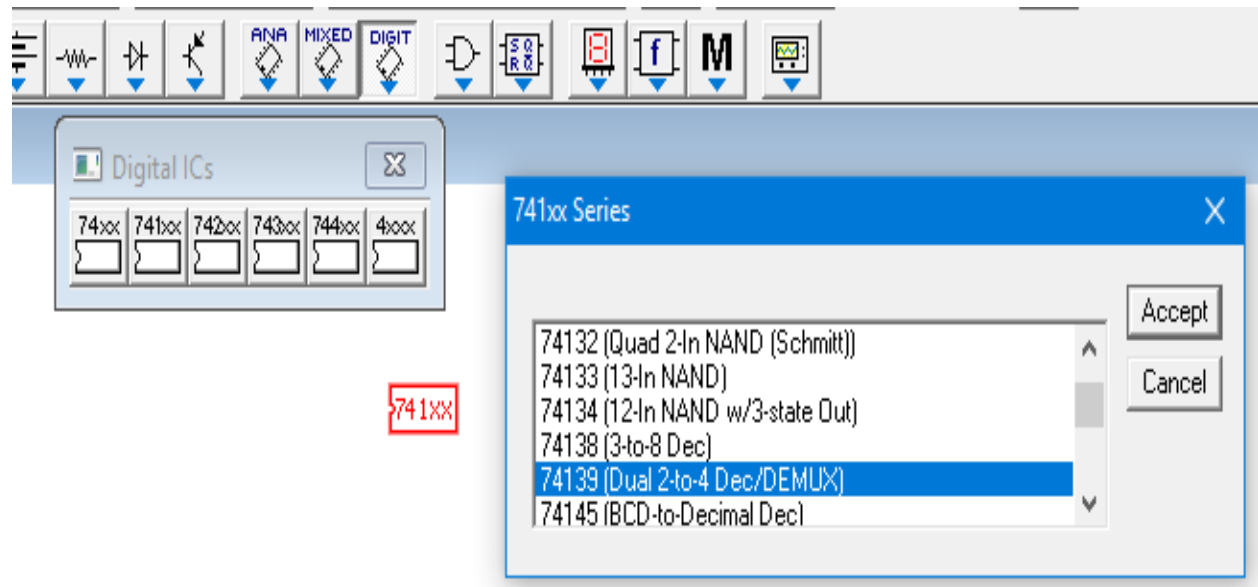
- Ground the MSB input of Decoder I.
- The LSB input of Decoder I will act as the MSB for the 3 x 8 decoder. When its 0, output Y0 will be selected, which will enable decoder II, and when its 1, output Y1 will be selected and decoder II will be enabled.
- Connect the LSB input of decoder II with the LSB input of decoder III.
- Connect the MSB input of decoder II with the MSB input of decoder III.

LAB TASKS:

TASK-I: Design a 3 x 8 decoder from three 2 x 4 decoders:

On EWB, design a 3 x 8 decoder using three 2 x 4 decoders and fill the table below.

On the toolbar, click on the  digital ICs button. From the toolbox, drag 741xx digital IC on to the workspace and choose your desired IC from the list, as shown below.



Inputs			Outputs							
A	B	C	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

OEL - I

IMPLEMENTATION OF HIGHER ORDER MULTIPLEXERS

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____: Total Marks: _____

Course Instructor: _____

OEL - II

FUNCTION IMPLEMENTATION USING COMBINATIONAL CIRCUITS

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____

OEL - III

FUNCTION IMPLEMENTATION USING SEQUENTIAL CIRCUITS

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : **Total Marks**: _____

Course Instructor: _____

OEL-IV

SEMESTER PROJECT

OBJECTIVE:

- To implement the knowledge you gained during the semester about digital logic designs in a creative manner.

INTRODUCTION:


Group projects reinforce skills that are relevant to both group and individual work. Some of the benefits of group projects are listed below.


- Breaking complex tasks into parts and steps.
- Planning and managing time.
- Refining understanding through discussion and explanation.
- Giving and receiving feedback on performance.
- Developing stronger communication skills.
- Sharing diverse perspectives.

PROJECT'S TITLE:


--

PROJECT'S INTRODUCTION:

  A large, empty rectangular box with a thin black border, intended for the project's introduction. It occupies the majority of the page below the header.



PROJECT'S LOGIC DIAGRAM:

 

CONCLUSIONS:

NAMES OF GROUP MEMBERS:

Laboratory Assessment

Student Name: _____ Reg. No.: _____

Criteria	Allocated Marks	Learning Level				Obtained Marks (P)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Psychomotor (evaluated during the experiment)	50%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (A)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Affective (evaluated during the Lab)	20%					

Criteria	Allocated Marks	Learning Level				Obtained Marks (C)
		Poor 40%	Good 50-60%	Very Good 70-80%	Excellent 90-100%	
Cognitive (evaluated on report submission)	30%					

Obtained Marks = $(0.5 \times P) + (0.2 \times A) + (0.3 \times C) =$ _____ : Total Marks: _____

Course Instructor: _____